

RAJSHAHI UNIVERSITY OF ENGINEERING AND TECHNOLOGY

Course no: CSE 2204

Course Title : Sessional Based on CSE 2203

Submitted to:

Dr.Boshir Ahmed,

Professor ,

Department of Computer
Science and Engineering
,RUET.

Md Zahirul Islam,

Lecturer,

Department of Computer
Science and Engineering
,RUET.

Submitted by:

Md Al Amin Tokder

Shoukhin ,

Roll: 1803078, Section: B

Department of Computer
Science and Engineering,
Rajshahi University of
Engineering and
Technology

Experiment no:5.1.1

Experiment name: Verify the Half Adder Circuit (implementing by basic logic gates)

Objectives :


- To learn about Half Adder Circuit
- Implement it by using basic gates
- Draw the truth table and verify the output result

Theory:

A half adder is an electronic circuit that performs the addition of two single binary digits and provides the output plus a carry value. It has two inputs called A and B and two outputs S(sum), and C(carry). In this experiment, we use basic gates including AND, OR, and NOT gate (without using XOR) to implement half adder.

Experimental result analysis:

1.Circuit Diagram:

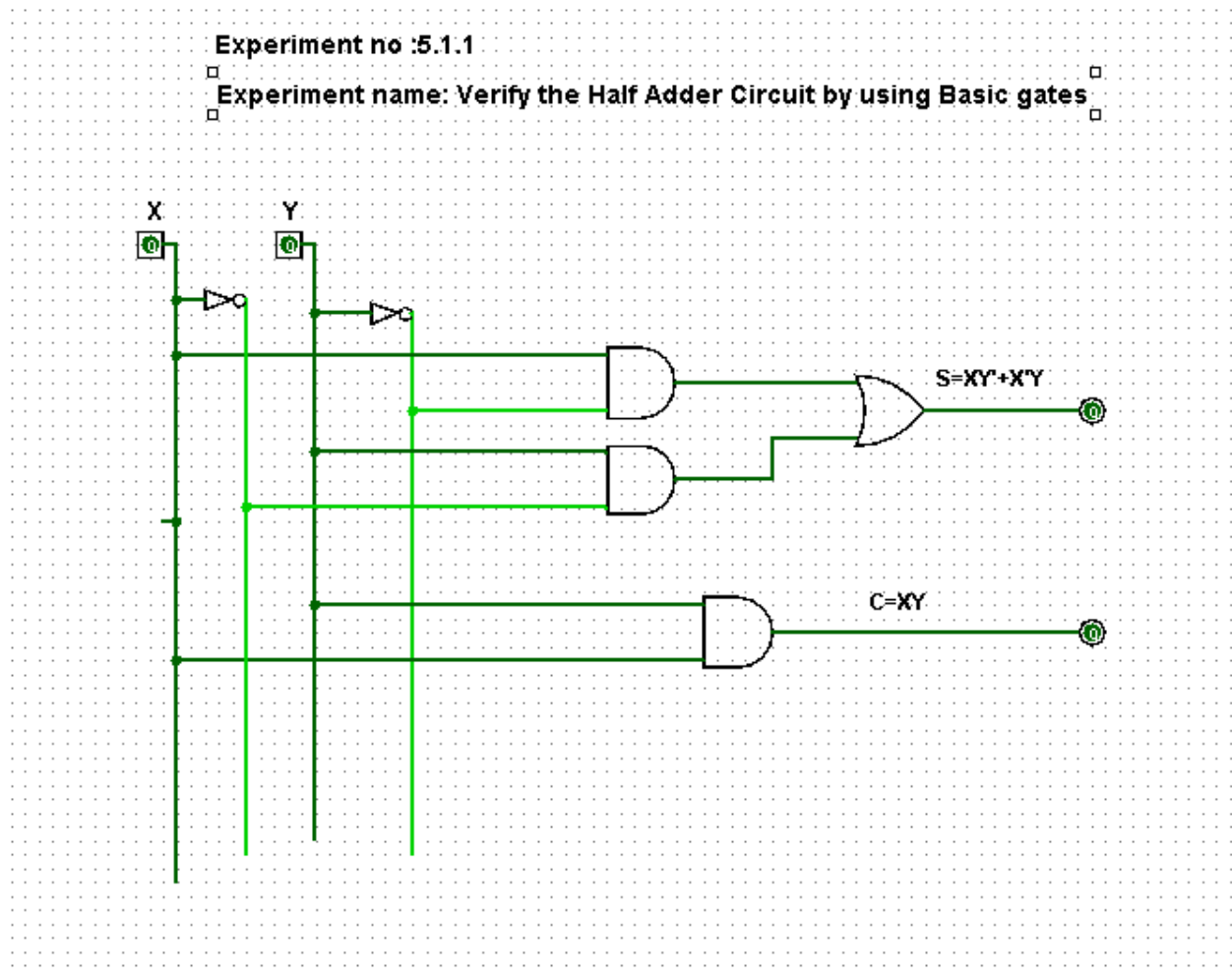

2.Truth Table:

X	Y	S(sum)	C(carry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Conclusion:

This half adder gate is implemented through logisim software with basic logic gate .By analyzing circuit I get a truth table which is similar the original half adder circuit truth table .That means the experiment finished successfully.

Experiment no:5.1.2

Experiment name: Verify the Half Adder Circuit (implementing by XOR gate)

Objectives :


- To learn about Half Adder Circuit
- Implement it by using XOR gate
- Draw the truth table and verify the output result

Theory:

A half adder is an electronic circuit that performs the addition of two single binary digits and provides the output plus a carry value. It has two inputs called A and B and two outputs S(sum), and C(carry). In this experiment, we use basic gates (AND, OR, NOT) and XOR gate to implement a half adder.

Experimental result analysis:

1.Circuit Diagram:

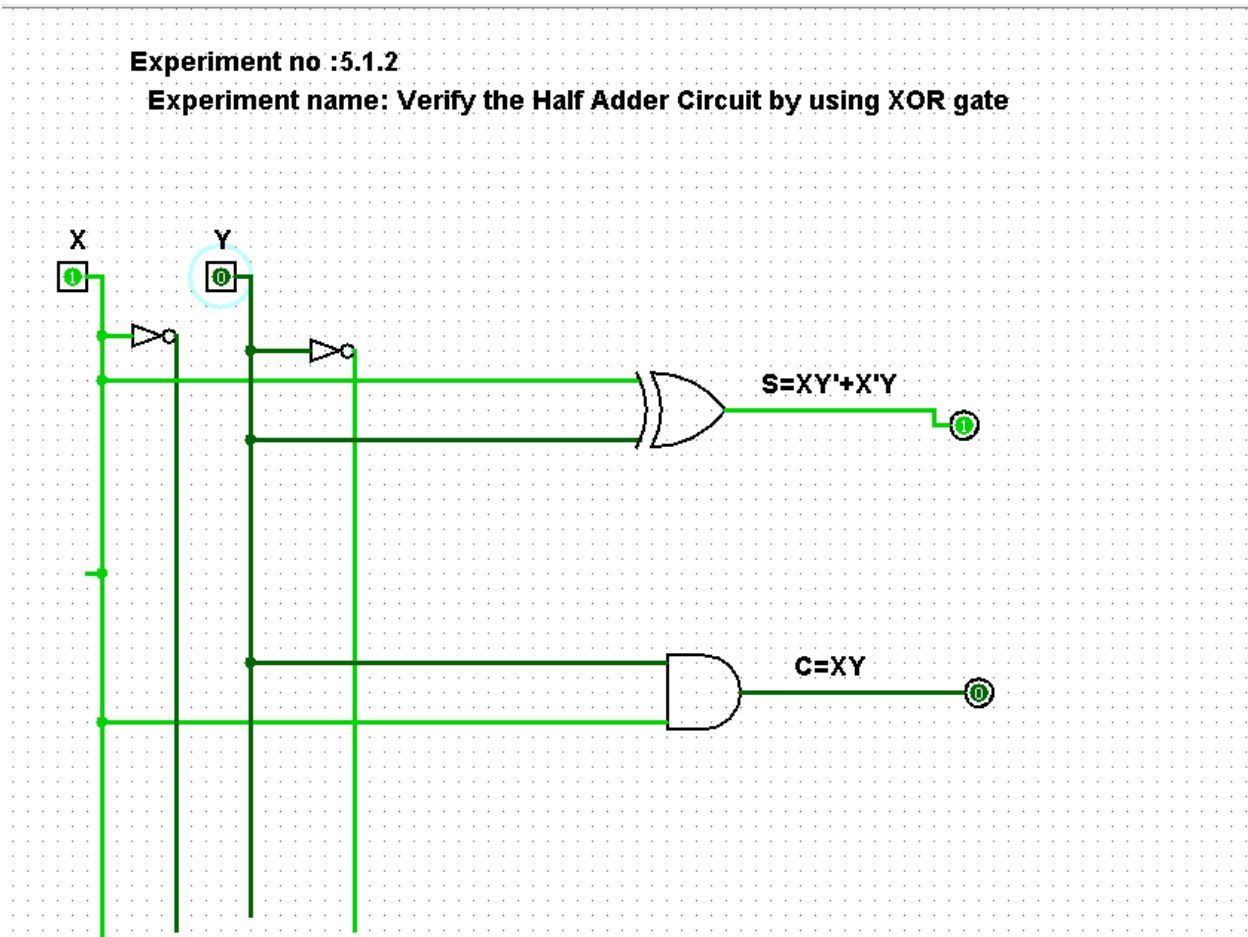

2.Truth Table:

X	Y	S(sum)	C(carry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Conclusion:

This half adder gate is implemented through logisim software with XOR gate .

By analyzing circuit I get a truth table which is similar the original half adder circuit truth table .That means the experiment finished successfully.

Experiment no:5.2.1

Experiment name: Verify the Full Adder Circuit(Implement by basic logic gates)

Objectives :

- To learn about Full Adder Circuit
- Implement it by using basic gates
- Draw the truth table and verify the output result

Theory:

A Full adder is an electronic circuit that performs the addition three single binary digits and provide the output plus a carry value . It has three inputs called A ,B and C and two outputs S(sum),and C(carry).From Sum of Product equation ,we implement the full adder circuit .

The SOP equation is,


$$S=X'Y'Z+X'YZ'+XY'Z'+XYZ$$

and

$$C=XY+YZ+ZX$$

Experimental result analysis:

1.Circuit Diagram:

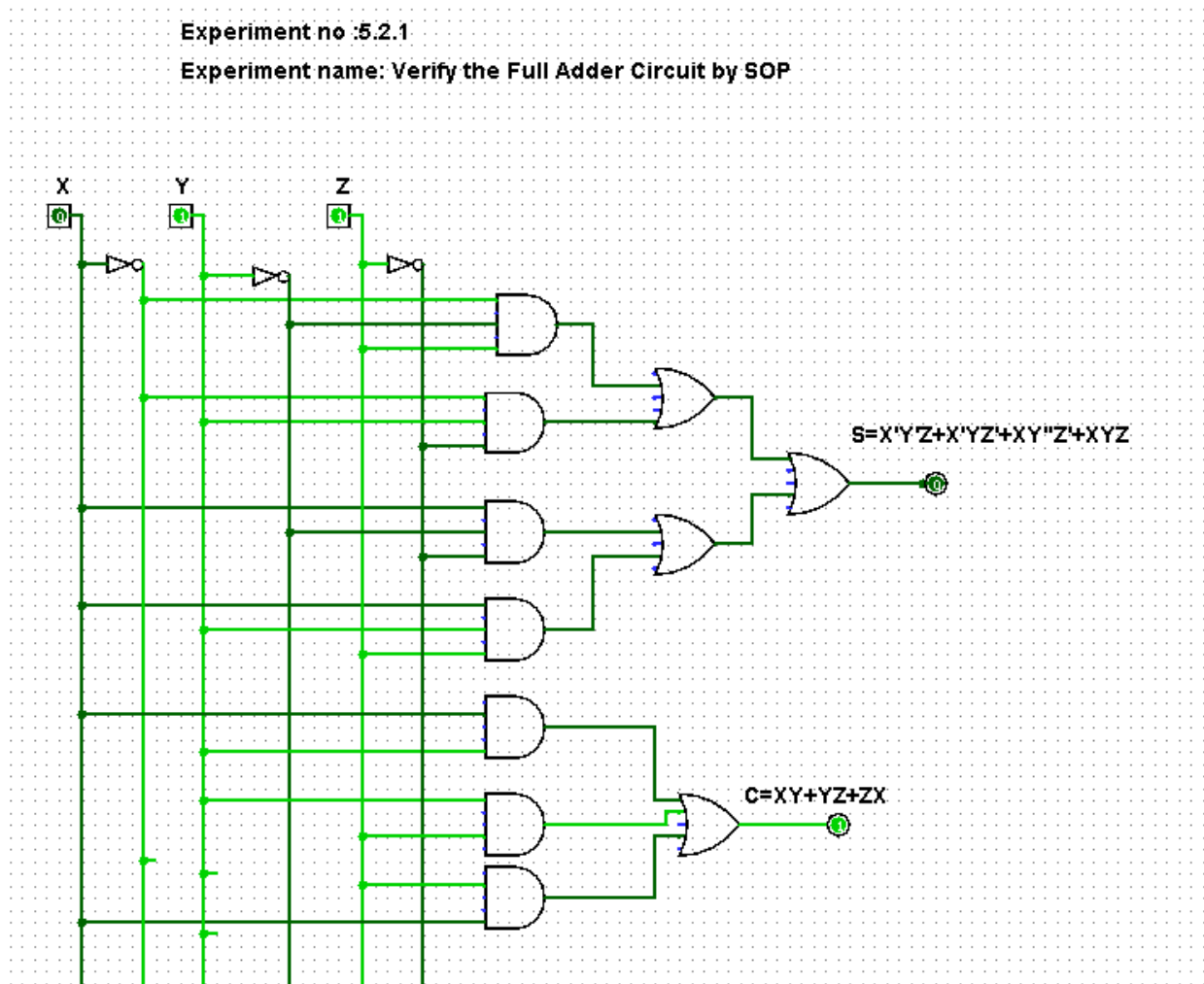

2.Truth Table:

X	Y	Z	S(sum)	C(carry)
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Conclusion:

This Full Adder gate is implemented through logisim software with basic logic gate .By analyzing circuit I get a truth table which is similar the original full adder circuit truth table .Thus the experiment finished successfully.

Experiment no:5.2.2

Experiment name: Verify the Full Adder Circuit(Implement by XOR gates)

Objectives :

- To learn about Full Adder Circuit
- Implement it by using XOR gate
- Draw the truth table and verify the output result

Theory:

A Full adder is an electronic circuit that performs the addition three single binary digits and provide the output plus a carry value . It has three inputs called A ,B and C and two outputs S(sum),and C(carry).

The SOP equation is,

$$S=X'Y'Z+X'YZ'+XY'Z'+XYZ$$

$$=Z(X'Y'+XY)+Z'(X'Y+XY')$$

$$=Z(X\oplus Y)'+Z'(X\oplus Y)$$

$$= (X\oplus Y\oplus Z)$$

and


$$C=X'YZ+XY'Z+XYZ'+XYZ$$

$$=X'YZ+XYZ+XY'Z+XYZ+XYZ'+XYZ$$

$$= (XY+YZ+ZX)$$

Experimental result analysis:

1.Circuit Diagram:

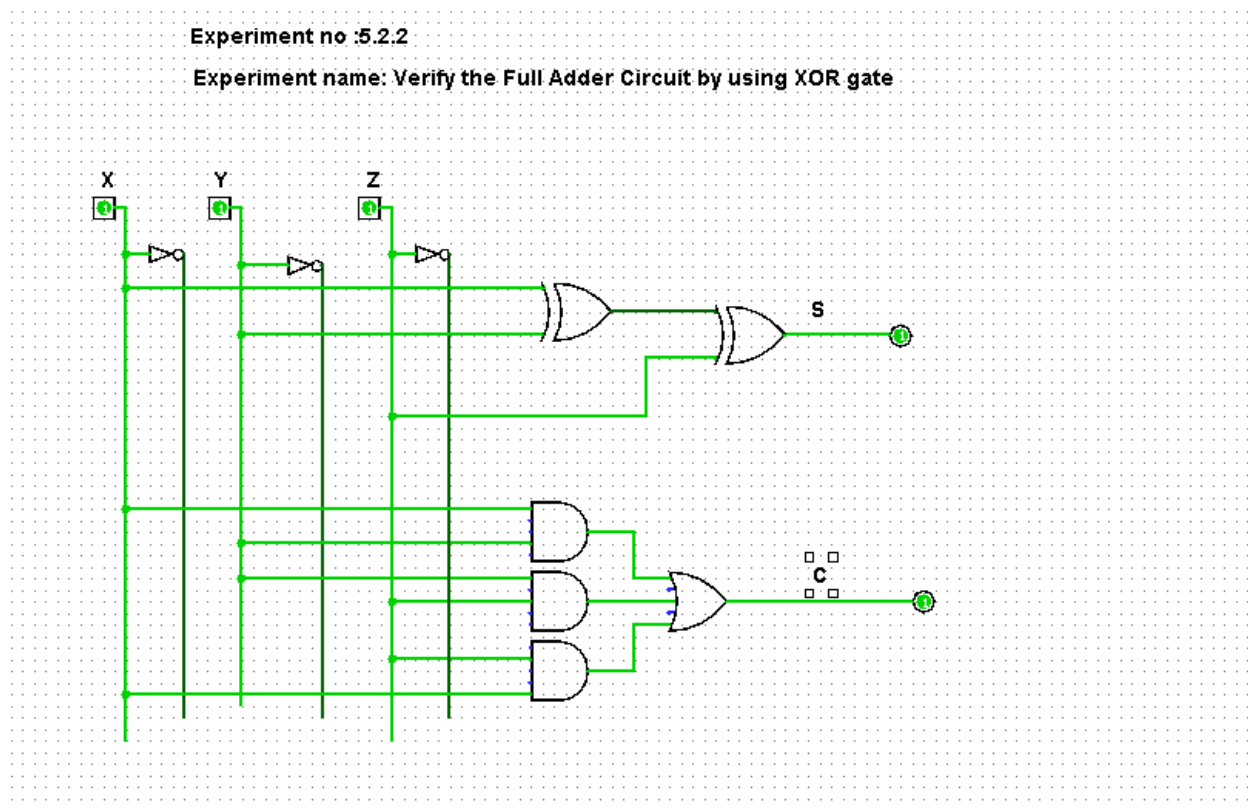

2.Truth Table:

X	Y	Z	S(sum)	C(carry)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Conclusion:

This Full Adder gate is implemented through logisim software with XOR gate .

By analyzing circuit I get a truth table which is similar the original full adder circuit truth table .Thus the experiment finished successfully.

Experiment no:5.3

Experiment name: Implement the Full Adder circuit by using Half Adder Circuit and verify the result

Objectives :

- To learn about Full Adder Circuit
- Implement it by using half adder circuit
- Draw the truth table and verify the output result

Theory:


A Full adder is an electronic circuit that performs the addition three single binary digits and provide the output plus a carry value . It has three inputs called A ,B and C and two outputs S(sum),and C(carry).We can implement full adder circuit by using two half adder circuit and a OR gate .

Experimental result analysis:

 1.Circuit Diagram:

Experiment no :5.3

Experiment name: Implement the Full Adder circuit by Half adder circuit and verify the result



2.Truth Table:

X	Y	Z	S(sum)	C(carry)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Conclusion:

This Full Adder gate is implemented through logisim software with two half adder circuit .

By analyzing circuit I get a truth table which is similar the original full adder circuit truth table .Thus the experiment finished successfully.